



Swakeup

PROJECT REPORT

within the lecture of
Microcontroller Programming

at Uppsala University
in the Departement of Information Technology

Elmar van Rijnsouw (elmarvanrijnsouw@hotmail.com) and Maximilian Stiefel (stiefel.maximilian@online.de)
Deadline: 2017-03-10 24:00

Processing Period:
Supervisor:

December 2016 - March 2017
Uwe Zimmermann (uwe.zimmermann@angstrom.uu.se)

Contents

| | | |
|----------|---|-----------|
| 1 | Introduction | 1 |
| 1.1 | Idea | 1 |
| 1.2 | Sytem Overview | 1 |
| 2 | Hardware | 3 |
| 2.1 | Logic Board | 3 |
| 2.2 | Power Board | 3 |
| 2.2.1 | Microcontroller Power Supply | 3 |
| 2.2.2 | Designated USB Charging Port | 3 |
| 2.2.3 | HW Debugging | 3 |
| 2.2.4 | RGB LED Driver | 3 |
| 3 | Software | 5 |
| 3.1 | Code Structure | 5 |
| 3.2 | Operating System | 5 |
| 3.3 | Realization | 5 |
| 4 | Status Quo and Outlook | 6 |
| 4.1 | What works? What does not work? | 6 |
| 4.2 | Outlook | 6 |
| A | Schematics Power Board | IV |

List of Figures

| | | |
|-----|---|---|
| 1.1 | Blockdiagram of the Swakeup wakeup light. | 1 |
|-----|---|---|

List of Tables

| | | |
|-----|---|---|
| 4.1 | Hardware Overview: What works? What does not? | 6 |
| 4.2 | Software Overview: What works? What does not? | 6 |

1 Introduction

Idea

It is a well-known fact, that it is quite dark in Sweden in the winter. In a strong winter every source of light is a source of happiness. This wakeup light, which is based on a strong light source (10 W RGB LED), is able to give one the optimal start into a dark winter day. The *Swakeup* (from engl. "Swedish Wakeup Light") is communicating to the user through the light. It does not simply wake one up, but also gives one information about Facebook, latest mails, calendar and weather. The user interface consists besides of a big LED of an OLED screen. *Swakeup* is also part of the *IoT* as it has the ability to communicate via *IEEE 802.11*. This of course enables a lot of possibilities e.g. connecting your phone to the wakeup light. A lot of effort has been put into the designing maxim, that everything should be as small as possible. The whole electronics fit on an base area of 5 cm x 4 cm. So the *Swakeup* fits smoothly on the bedside table. And honestly: What is the last thing you are doing before you go to sleep? Right! You look on your phone. That is why *Swakeup* comes with a USB charger for your e.g. phone as well.

Sytem Overview

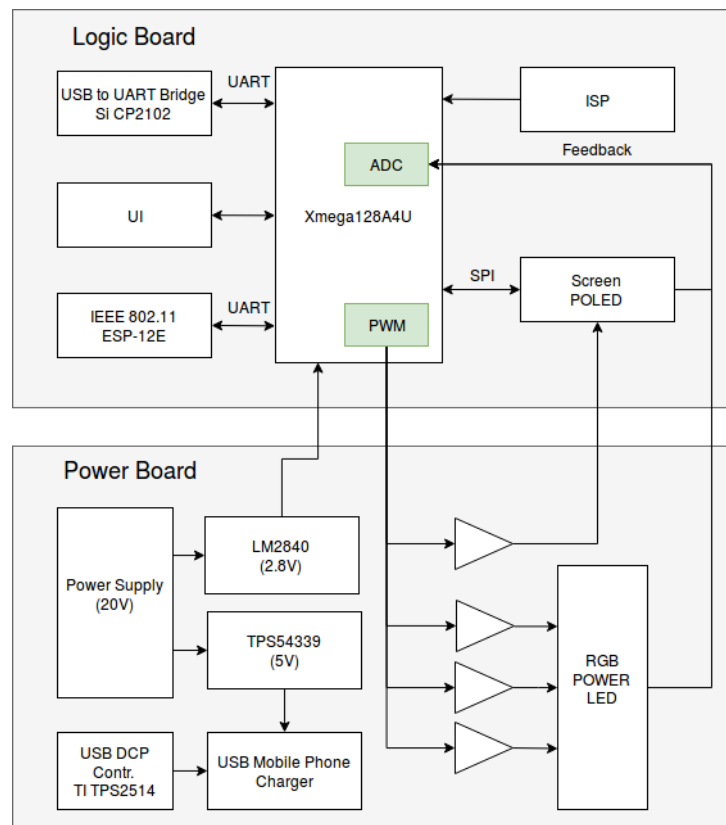


Figure 1.1: Blockdiagram of the Swakeup wakeup light.

In fig. 1.2 the actual system architecture from an abstract point of view is displayed. One can clearly see, that the system is divided into two physical boards. The logic board consists of the μC , a serial connection infrastructure, an OLED screen, an *IEEE 802.11* module, a ISP programming infrastructure and some LEDs/a button (UI).

The power board takes the 20 V input of a low-cost power supply and breaks it down to 2.8 V (Vcc), 5 V for phone charging and the power which is needed for the RGB LED.

The partitioning of the system functionalities on two boards has a bunch of advantages: Two people worked on this project, so each could develop a PCB; It is quite common to separate signals from power lines out of EMI reasons; There was simply not enough space on one two-layer board for the whole system keeping a base area of 5 cm x 4 cm.

The two boards are connected together through four headers. By these headers an electrical and mechanical connection is maintained. The headers allow a feedback from the LED driver on the power board to the logic board (ADC). Also the control variable (PWM) comes via the headers from the μC to the LED driver. The 2.8 V Vcc is produced and regulated on the power board and is also available at one header. Another voltage available from one header is the OLED driver voltage.

2 Hardware

Logic Board

Power Board

The board design has been made in *KiCAD*. *Git* was used for version control. In the schematics (Appendix A) one can see that the whole board consists of three main building blocks: Connectors, a LED driver with feedback and two step-down converters. A part of the LED driver is also "abused" to drive the OLED.

Microcontroller Power Supply

There are two step-down converter ICs on the power board. It is the LM2840 which in combination with a simple voltage divider ensures the 2.8 V for Vcc. All step-down converters use the same inductor with a value of 33 μ H. It is a low-cost, quite small, shielded inductor which is ment to be used for switching power supplies. Moreover all step-down converters are enhanced with a SMD schottky diode and a of course SMD capacitor for smoothing the output signal. As it is good practice to do so all ICs are making use of decoupling capacitors.

Designated USB Charging Port

For charging ones phone the TS30012, another step-down converter IC, is used. The feedback voltage divider of this IC is already integrated and does not need to be provided externally as the IC provides fixed 5 V output. The output is connected to a USB connector type A. This IC can deliver up to 2 A. An interesting feature of the phone charging circuitry on the power board is the "Dedicated Charging Port" (DCP) functionality. The TPS2514 is a small, easy-to-use, 6-pin component, which complies to the USB standard and a majority of the minefield of proprietary standards to signal a DCP. What does that mean? Well this means, that if you connect your iPhone, it will know, that it can draw more than 100 mA, which is the minimum current provided by a normal USB 2.0 port. Otherwise the current drawn by the phone will be limited. The charging functionality can be turned on and off via a GPIO pin. The TS30012 comes in a QFN16 package (pad pitch of 0.5 mm) to save space.

HW Debugging

For testing purposes a lot of test points have been included into the design. Futhermore there are LEDs for different voltages (e.g. Vcc).

RGB LED Driver

The LED driver consists of an actual power electronics part and a feedback part. The idea is, that the voltage driven through the three color channels of the RGB LED can be controlled by software (PID controller). In the power electronics part there are three analog circuits. Each circuit mainly consists of a p-channel MOSFET, which is switched by a NPN bipolar transistor. This bipolar transistor gets its input signal from the μ Processor (PWM). By pulling the 20 V to GND the PMOS "sees" a negative gate-to-source voltage and opens. The additional bipolar transistor ensures, that the gate-source capacity is charged fastly as soon as the PWM NPN blocks. In this case the base is pulled up via 10 k Ω to 20 V and as long as the collector (which has the same potential as the gate of the PMOS) does not also have 20 V the NPN keeps pumping charge into the gate-source capacity. The simple silicon diode ensures that

the gate-charging NPN has no effect as soon as the PWM NPN opens. The rest of the circuit is again a standard step-down converter. At the output of every single color channel power circuit one can see a shunt resistor of $0.1\ \Omega$. This shunt resistor is combined with a simple low-pass filter. The feedback signal is amplified by a differential amplifier which comes after the filter. The signal is supposed to be between 0 V and 1 V (if the internal reference voltage is used). By doing so one can use all bits of the ADC and therefore suppress quantization noise.

So as there are three color channels (red, green and blue) one needs three operational amplifiers. Hence the LM324QT, which provides four operational amplifiers, has been chosen. Of course QFN16 was selected as the package once more to save even more space. An additional operational amplifier was now ready to be used as a digital-analog converter to drive the OLED screen (this was referred to earlier as "abuse"). For this reason a low-pass filter is attached to the input of the fourth opamp. Apart from that the opamp is configured just like a standard non-inverting amplifier. By software the OLED screen brightness is steerable. The feedback from the OLED is generated by a voltage divider.

3 Software

Code Structure

Operating System

Realization

4 Status Quo and Outlook

What works? What does not work?

The hardware right now is in revision 2.0. There has been one revision before the current one. This revision has been fabricated in january 2017 and the design process began in november 2016. There were some mistakes on the first hardware revision, which were not fixable so easily, especially because of the fact, that everything is quite small. Table 4.1 gives an overview of the current satus of the hardware.

| HW Block | Working | Problem |
|-----------------|---------|----------------------------|
| USB Charging | ✓ | |
| OLED Driver | ✓ | |
| Vcc for μC | ✓ | |
| IEEE 802.11 | ✓ | |
| USB2UART | ✓ | |
| LED Driver | | Wrong footprint assignment |
| Crystal | | Wrong pin assignment |
| USB DCP | | Further tests necessary |

Table 4.1: Hardware Overview: What works? What does not?

Table 4.2 deals with an overview about the status of the software.

| SW Block | Working | Problem |
|------------|---------|---------|
| UART | ✓ | |
| SPI | ✓ | |
| EPROM | ✓ | |
| Timer | ✓ | |
| ADC | | |
| PWM | | |
| ESP8266 | ✓ | |
| Terminal | ✓ | |
| SEP525F | ✓ | |
| Wifi | | |
| Command | ✓ | |
| Log | ✓ | |
| Screen | ✓ | |
| Timekeeper | ✓ | |
| Controller | | |
| Core | ✓ | |
| Weather | ✓ | |
| Clock | ✓ | |
| Social | | |


Table 4.2: Software Overview: What works? What does not?

Outlook


Hopefully the LED driver will work with the next revision. The new boards have not arrived until the deadline. As soon as the hardware is working, the controllers will be implemented in software.

Additional functionality will be implemented e.g. connecting your calendar to the device and seeing your daily agenda when you wake up. Also there is no housing yet.

A Schematics Power Board


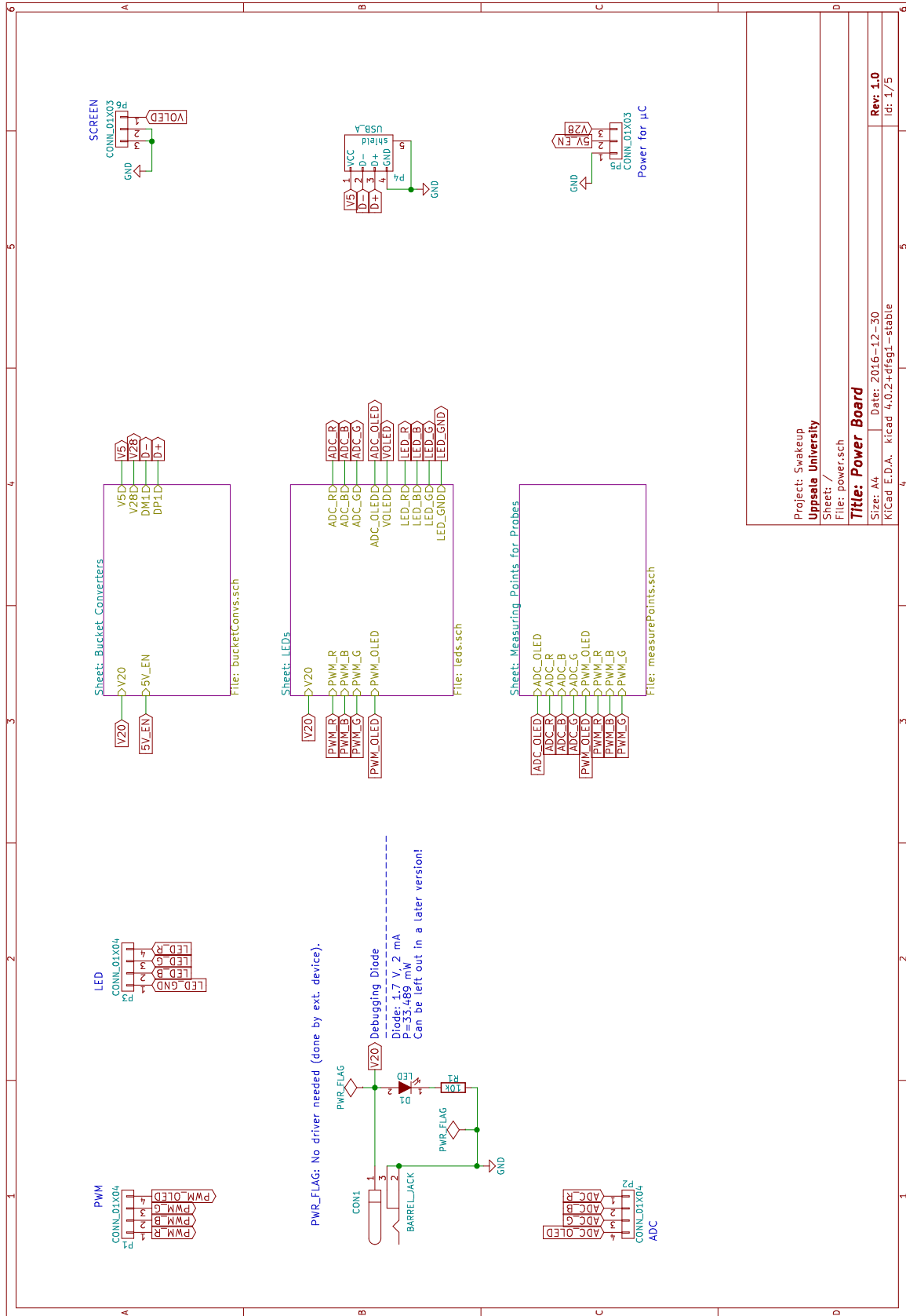


$$2.8 \text{ V for } \mu\text{C}$$
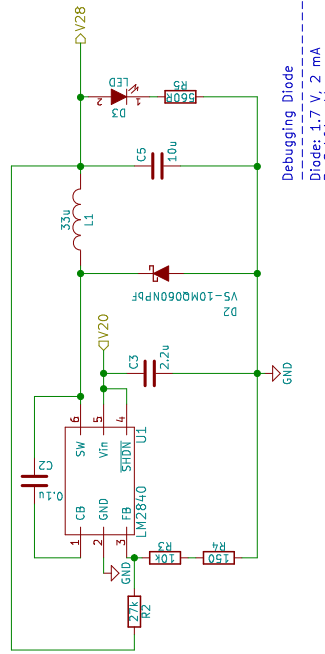
$$V_{\text{out}} = 0.765 \text{ V} \left(1 + \frac{27\text{k}\Omega}{10.15\text{k}\Omega} \right) = 2.8 \text{ V}$$


5V for Mobile Phone

Vout,max=5 V
Aout,max = 2A

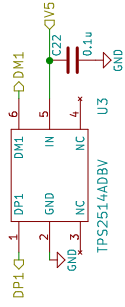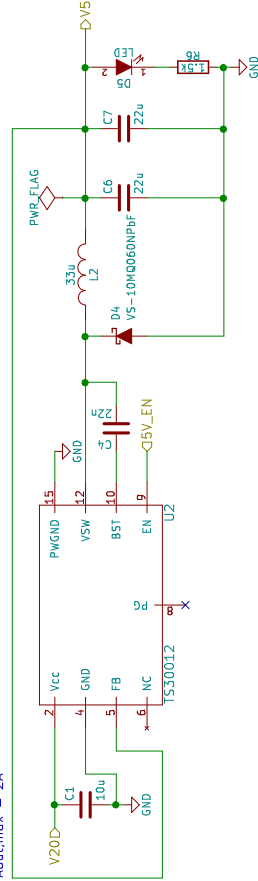

USB Dedicated Charging Port Control.

Simple S01-23-6 IC for detecting proprietary and open standards used by a device and providing the corresponding electrical signature at the data lines (voltage or impedance).

